

2.3.1 Cramer's rule and matrix model

Cramer's rule is used for the solution of linear equations by determinants. Let the system of linear equations in three unknown I_1, I_2 and I_3 are:

$$\begin{aligned}R_{11}I_1 + R_{12}I_2 + R_{13}I_3 &= V_1 \\R_{21}I_1 + R_{22}I_2 + R_{23}I_3 &= V_2 \\R_{31}I_1 + R_{32}I_2 + R_{33}I_3 &= V_3\end{aligned}$$

May be written in matrix form as:

$$\begin{pmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix}$$

Where R_{ii} = the total resistance of the i^{th} loop with +ve sign.

R_{ij} = common resistance between i^{th} loop and j^{th} loop with -ve sign.

Then by Cramer's rule, the solution of these simultaneous equations is given by:

$$I_1 = \frac{\Delta_1}{\Delta}, I_2 = \frac{\Delta_2}{\Delta} \text{ and } I_3 = \frac{\Delta_3}{\Delta}$$

Where,

$$\Delta = \begin{vmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{vmatrix}$$

$$\Delta_1 = \begin{vmatrix} V_1 & R_{12} & R_{13} \\ V_2 & R_{22} & R_{23} \\ V_3 & R_{32} & R_{33} \end{vmatrix}$$


$$\Delta_2 = \begin{vmatrix} R_{11} & V_1 & R_{13} \\ R_{21} & V_2 & R_{23} \\ R_{31} & V_3 & R_{33} \end{vmatrix} \text{ and}$$

$$\Delta_3 = \begin{vmatrix} R_{11} & R_{12} & V_1 \\ R_{21} & R_{22} & V_2 \\ R_{31} & R_{32} & V_3 \end{vmatrix}$$

Cramer's rule can be used for solving simultaneous equations if the numbers of unknown are more than two. This gives quick results.

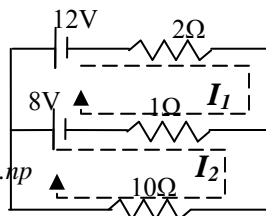Example: 2

Generate the matrix model for the circuit given below for the branch currents.



Ans:

$$\begin{pmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

Or

$$\begin{pmatrix} 2+1 & -1 \\ -1 & 10+1 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} -12+8 \\ -8 \end{pmatrix}$$

Or

$$\begin{pmatrix} 3 & -1 \\ -1 & 11 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} -4 \\ -8 \end{pmatrix}$$

Example: 3

Solve the following three simultaneous equations using Cramer's rule.

$$I_1 + 3I_2 + 4I_3 = 14$$

$$I_1 + 2I_2 + I_3 = 7$$

$$2I_1 + I_2 + 2I_3 = 2$$

Ans:

As explained earlier, the matrix model for the given circuit can be written in the form:

$$\begin{pmatrix} 1 & 3 & 4 \\ 1 & 2 & 1 \\ 2 & 1 & 2 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 14 \\ 7 \\ 2 \end{pmatrix}$$

$$\Delta = \begin{vmatrix} 1 & 3 & 4 \\ 1 & 2 & 1 \\ 2 & 1 & 2 \end{vmatrix} = 1(4-1) - 1(6-4) + 3(3-8) = -9$$

$$\Delta_1 = \begin{vmatrix} 14 & 3 & 4 \\ 7 & 2 & 1 \\ 2 & 1 & 2 \end{vmatrix} = 14(4-1) - 7(6-4) + 2(3-8) = 18$$

$$\Delta_2 = \begin{vmatrix} 1 & 14 & 4 \\ 1 & 7 & 1 \\ 2 & 2 & 2 \end{vmatrix} = 1(14-2) - 1(28-8) + 2(14-28) = -36$$

$$\Delta_3 = \begin{vmatrix} 1 & 3 & 14 \\ 1 & 2 & 7 \\ 2 & 1 & 2 \end{vmatrix} = 1(4-7) - 1(6-14) + 2(21-28) = -9$$

∴ According to Cramer's rule,

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{18}{-9} = -2A; I_2 = \frac{\Delta_2}{\Delta} = \frac{-36}{-9} = 4A; I_3 = \frac{\Delta_3}{\Delta} = \frac{-9}{-9} = 1A$$